

IIT Bombay

# Makerspace (MS101)

2024 (Spring)

EE-Lecture-10

## **Transistors as Switches**

Kushal Tuckley, Joseph John, PC Pandey, Dinesh K Sharma  
D Chakraborty, K Chatterjee, BG Fernandes, NS Shiradkar

# Transistors: Introduction

A transistor is a 3-terminal semiconductor device. It is used as a 2-port device with one terminal common between the input and output ports. It can be modelled as a 'dependent current source'.

## Commonly used types of Transistors

(a) **Bipolar Junction Transistor** (BJT)


(b) **Metal Oxide Field Effect Transistor** (MOSFET)

Type

Circuit Symbol

Simplified Signal Model

Bipolar Junction  
Transistor

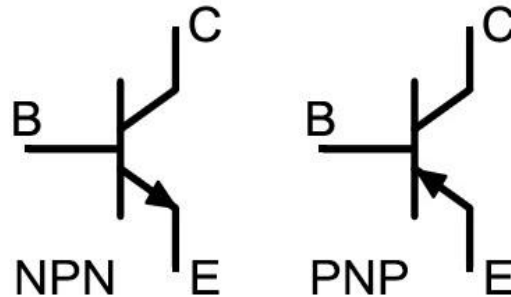


B: **Base**


C: **Collector**

E: **Emitter**

Common Emitter Configuration

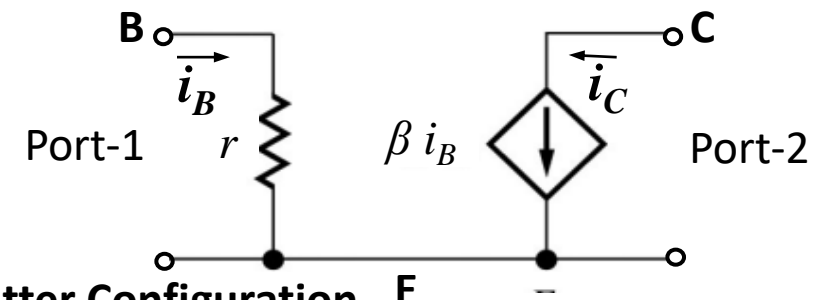

MOSFET  
(Enhancement mode)

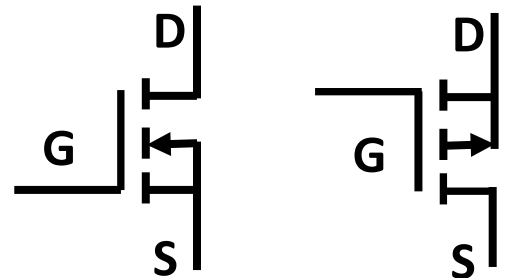

N Channel


P Channel

G: **Gate**


D: **Drain**

S: **Source**

Common Source Configuration

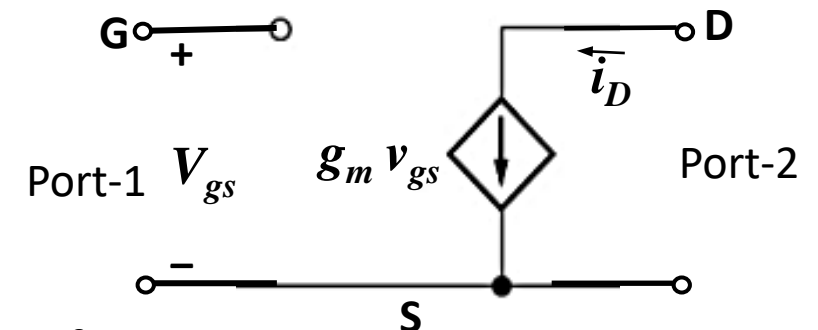


# Bipolar Junction Transistor (BJT)

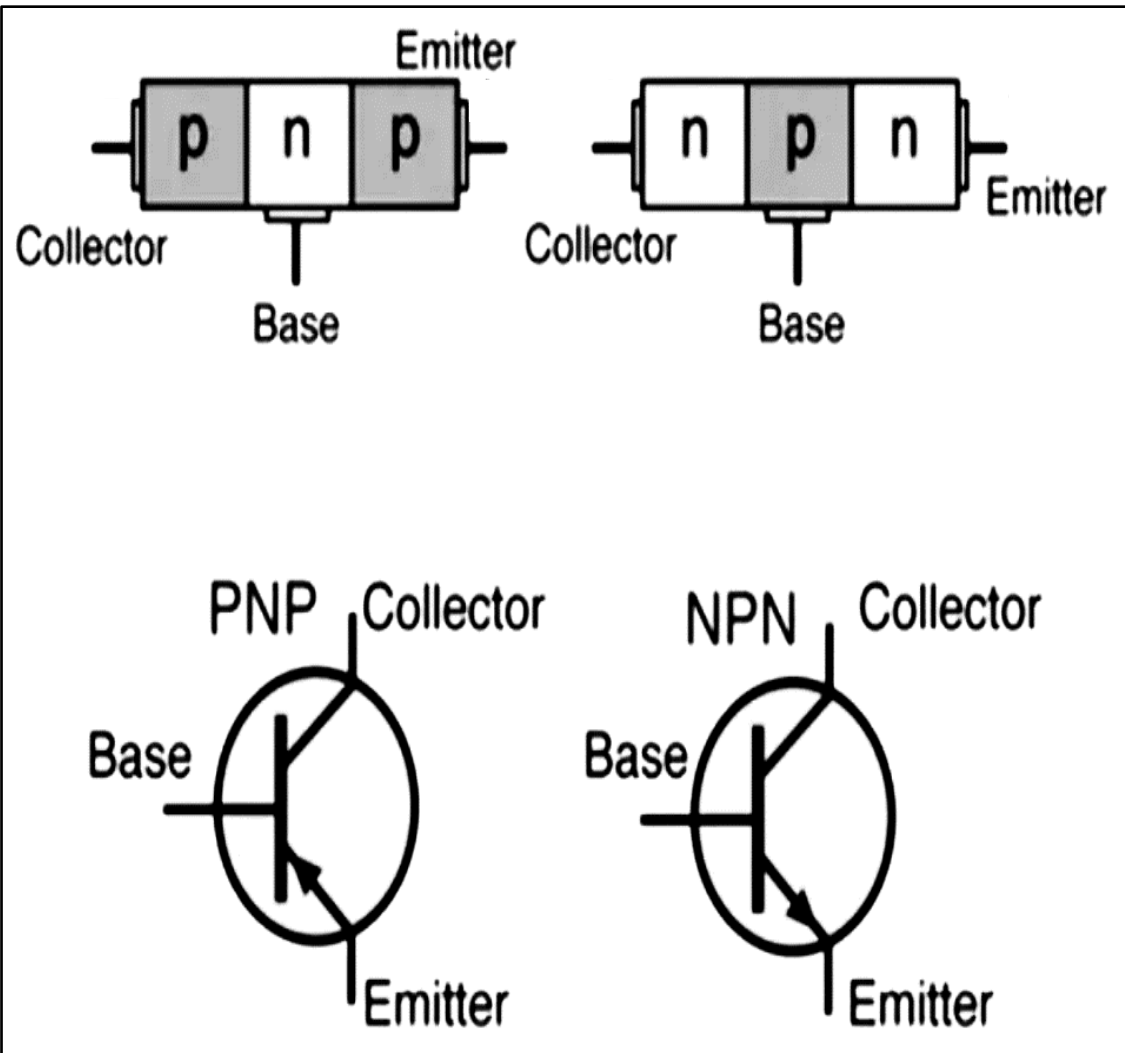


<b>Types</b>	NPN and PNP.
<b>Terminals</b>	Three terminals viz. emitter, base and collector.
<b>Controlling quantity</b>	BJT is a current controlled device Base current ( $I_B$ ) controls the Collector Current ( $I_C$ ).
Compared to MOSFETs, BJTs have lower input resistance ( $\approx 10\text{ k}\Omega$ to $1\text{ M}\Omega$ , in common emitter configuration) and hence consume more power from the input signal source.	

Input Resistance: BJTs < MOSFETs

# BJT Operation: Cricket Analogy

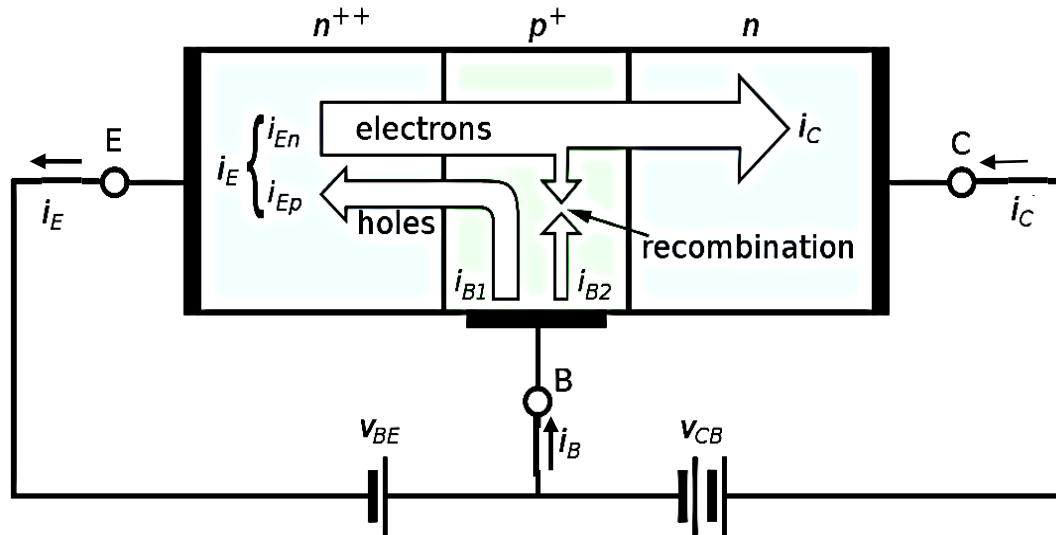

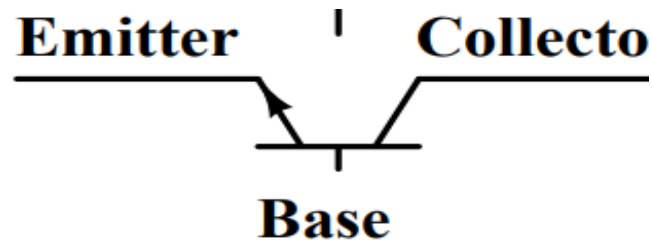
- The emitter is the bowler who shoots electrons into the base.
- The base is the batsman – a tail-ender who swings away, but connects with no more than 1 to 2% of the incoming balls (electrons).
- Most of the balls are collected by the wicket keeper – the collector.



- The base current (rare balls connected by the batsman) is a fraction of the emitter current and the collector current is almost equal to the emitter current.
- Thus the collector current is 50 to 100 times the base current. Ratio of collector current to the base current is the current gain of the transistor.

Ratio of the collector to the base current is current gain.


# BJT Operation: Current Flow

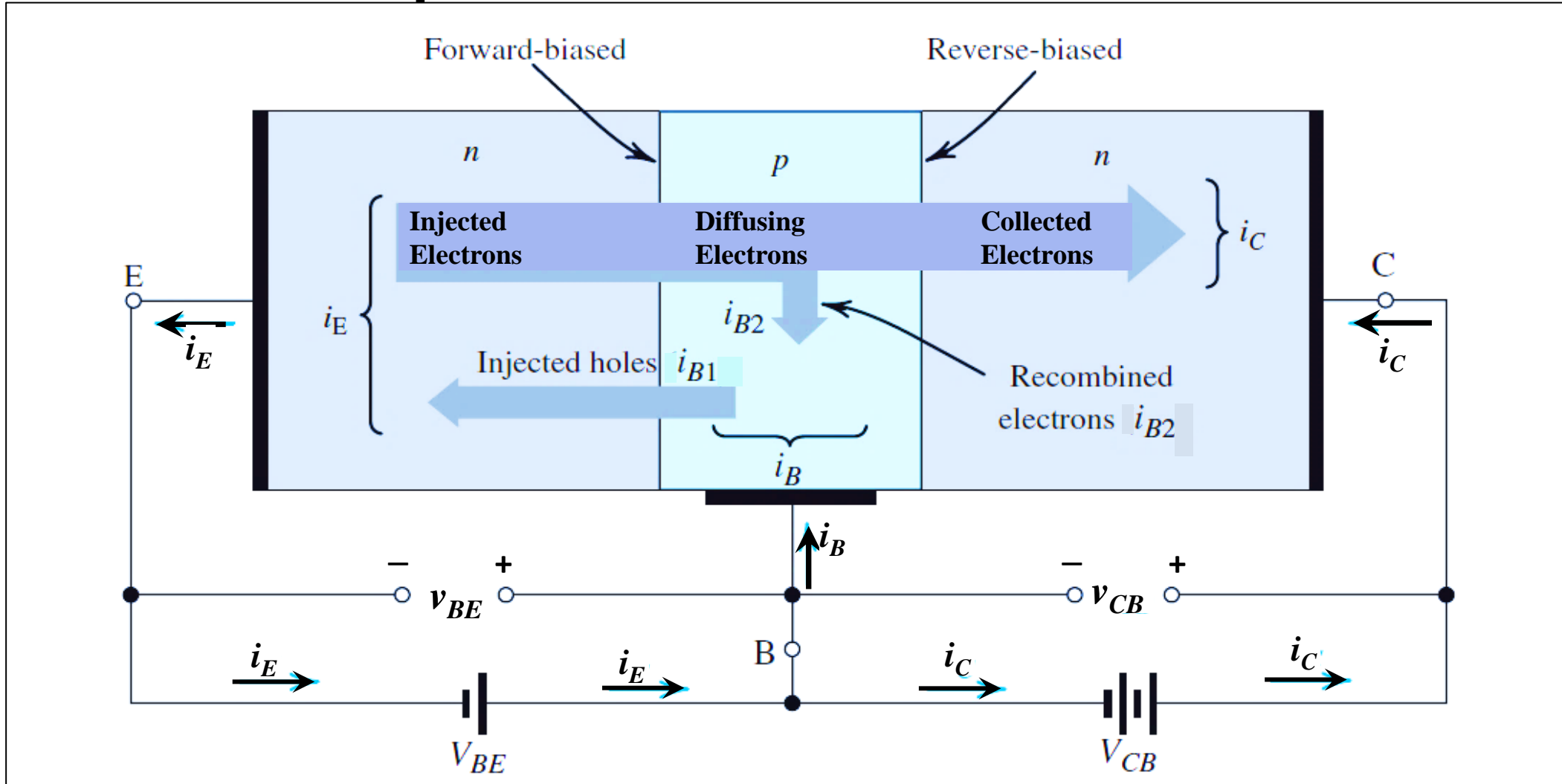

**Current flow in an NPN transistor biased in active mode (forward biased BE junction and reversed biased BC junction)**
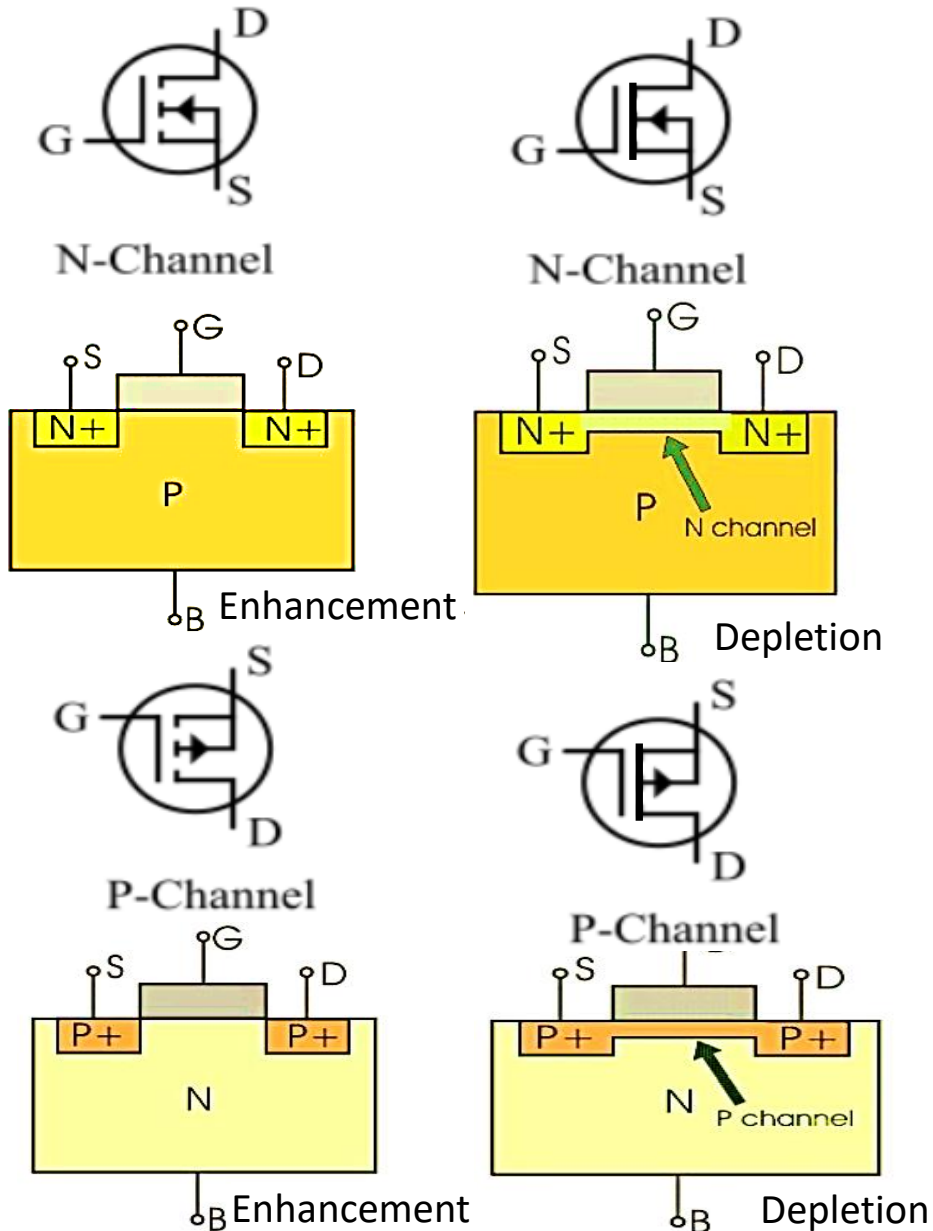
# Metal Oxide Field Effect Transistor (MOSFET)



MOSFETs are available in two Types → N-Channel and P-Channel. They are fabricated in two modes: Enhancement and Depletion.



MOSFET	
Types (4)	P-channel enhancement, P-channel depletion, N-channel enhancement, N-channel depletion.
Terminals (4)	Source (S), Drain (D), Gate (G), Substrate or body (B). B is often connected to S.
Controlling quantity	MOSFET is a voltage-controlled device. Gate-to-source voltage ( $V_{GS}$ ) controls drain-to-source current ( $I_{DS}$ ).
MOSFETs have high input resistance (10 M $\Omega$ to 100 M $\Omega$ , depending on configuration and circuit) and hence consume less power from the input signal source, compared to BJTs.	

# MOSFET Operation

## N- Channel Depletion mode MOSFET

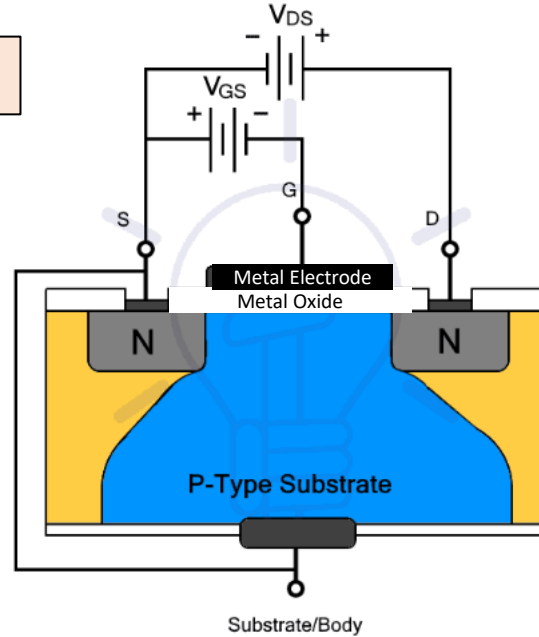
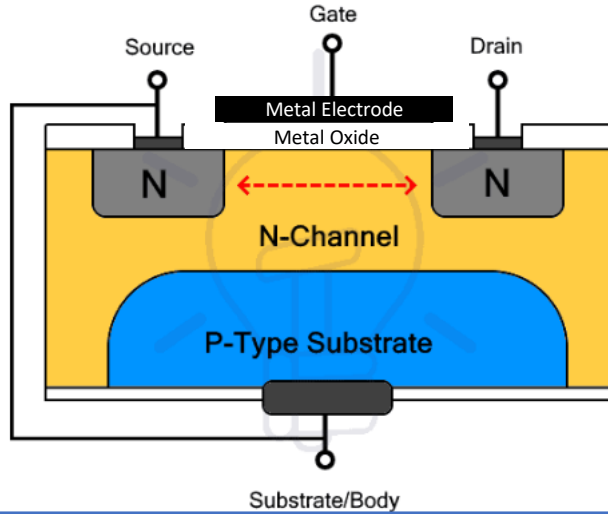


The MOSFET is said to be ON when current flows between Drain and Source

**Depletion mode:** Channel for drain-source current flow is available at  $V_{GS} = 0$ . The channel gets depleted for negative  $V_{GS}$ , and it is totally depleted for  $V_{GS}$  below the threshold voltage,  $V_{TH}$  (-ve for N-channel).

**Enhancement mode:** No channel is available at  $V_{GS} = 0$ . The channel for drain-source current flow is formed for  $V_{GS}$  above the threshold voltage,  $V_{TH}$  (+ve for N-channel).

## N- Channel Enhancement mode MOSFET

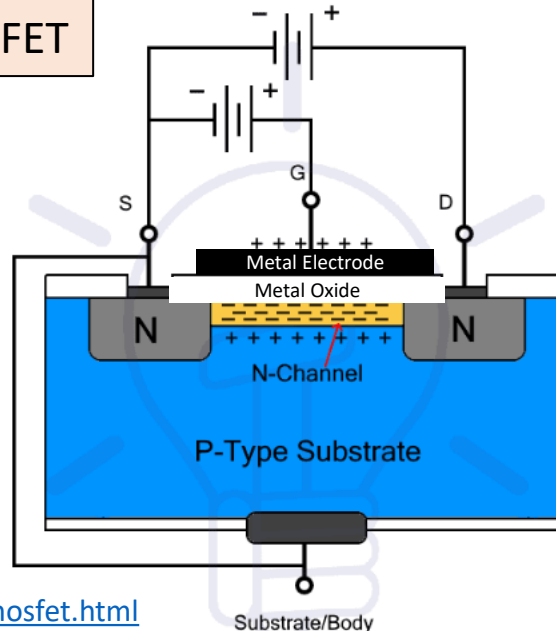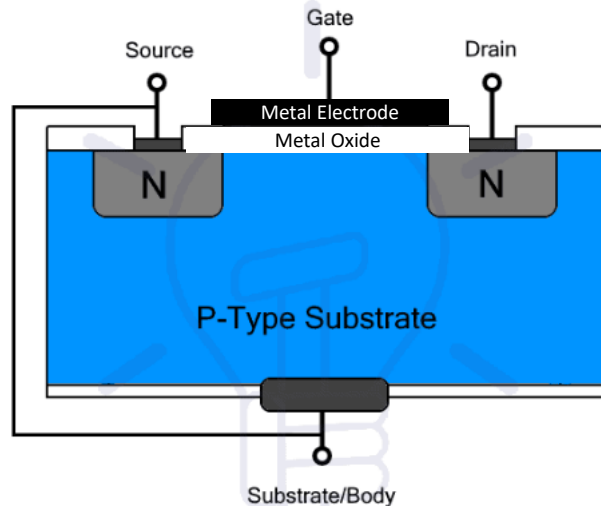

### MOSFET Type

### Condition for Switching

N – Channel Enhancement

OFF for  $V_{GS} < V_{TH}$  ( 0.6 to 1 V )

N - Channel Depletion

OFF for  $V_{GS} < V_{TH}$  ( - 1.3 to - 0.0 V )

P - Channel Enhancement


OFF for  $V_{GS} > V_{TH}$  ( - 1.0 to - 0.6 V )

P - Channel Depletion

OFF for  $V_{GS} > V_{TH}$  ( 0.0 to 1.3 V )



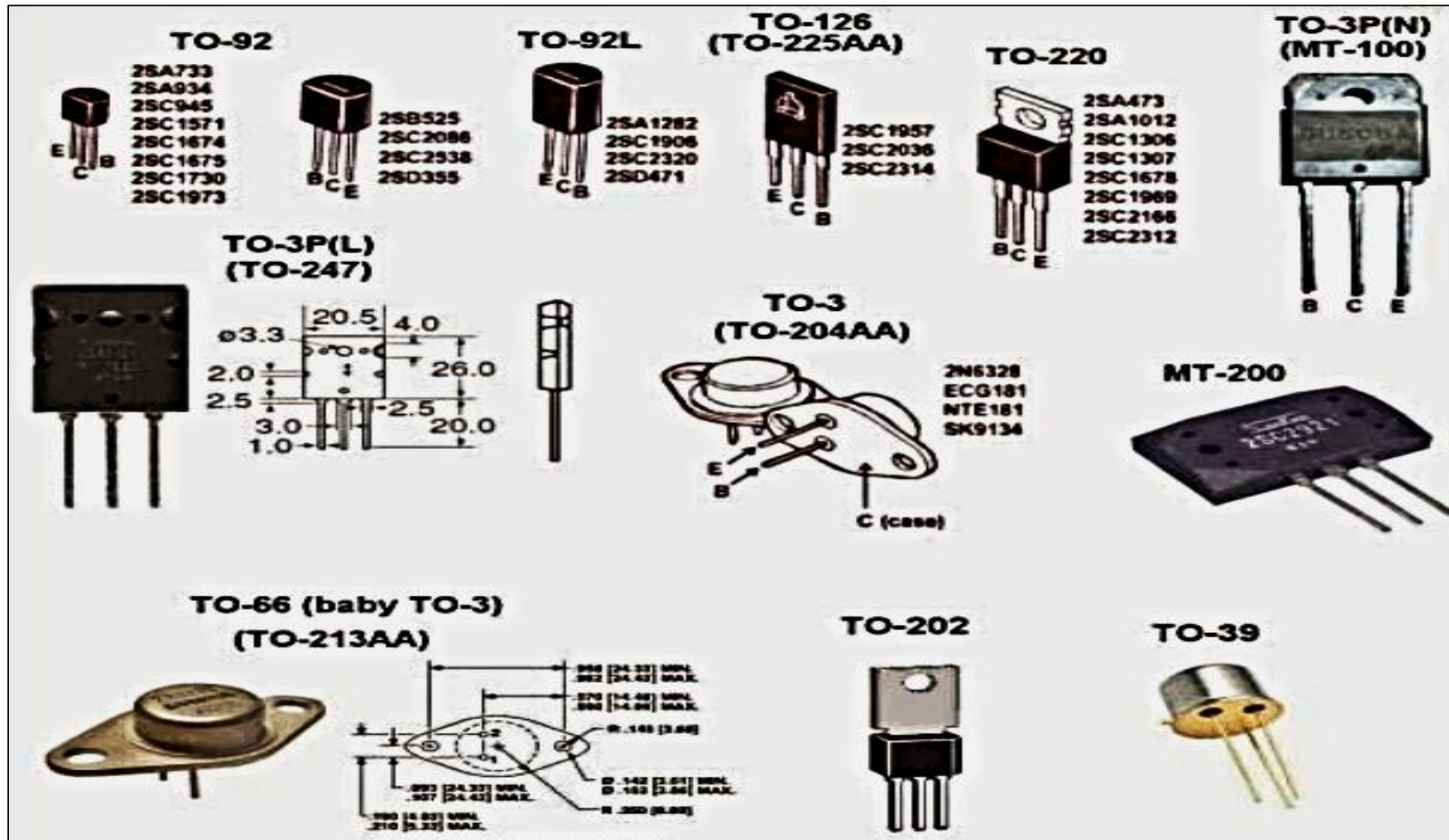
# Commercially Available Transistor Packages





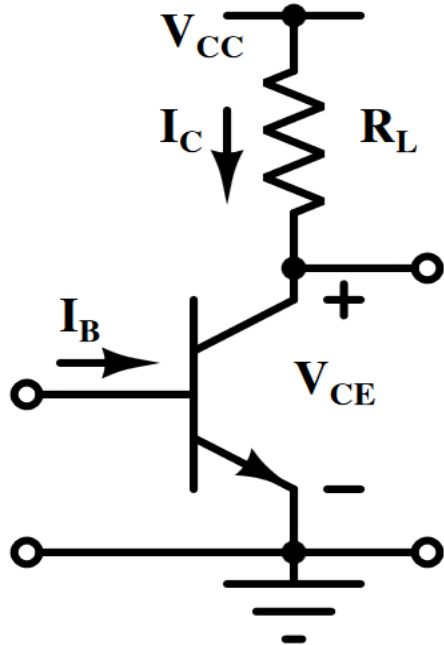
# Switching Characteristics of BJT Presented on $V_{CE}$ - $I_C$ Plane



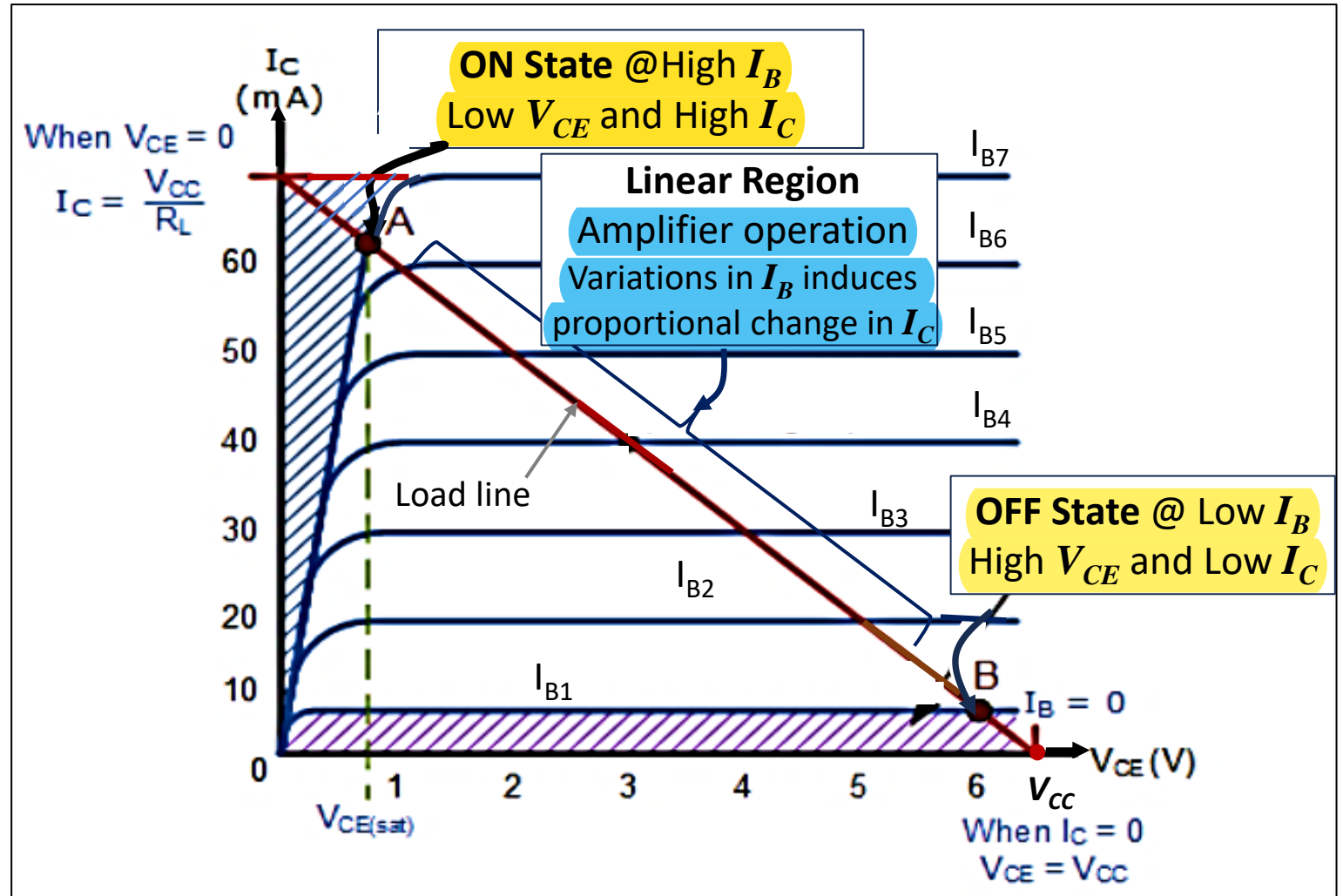BJT is switched ON or OFF by changing the base current ( $I_B$ )




Typical ' $V_{CE}$  -  $I_C$ ' characteristics for BJT

A & B are the operating points for the switching action


# Switching Characteristics of N-Channel Enhancement mode MOSFET
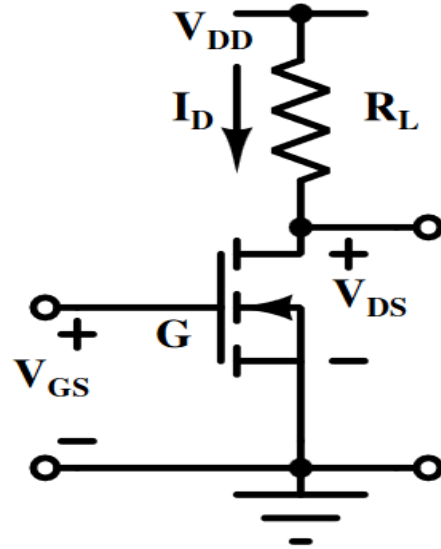
## (Presented On $V_{DS}-I_D$ Plane)

In BJT current controls output current  
In MOSFET voltage controls output current




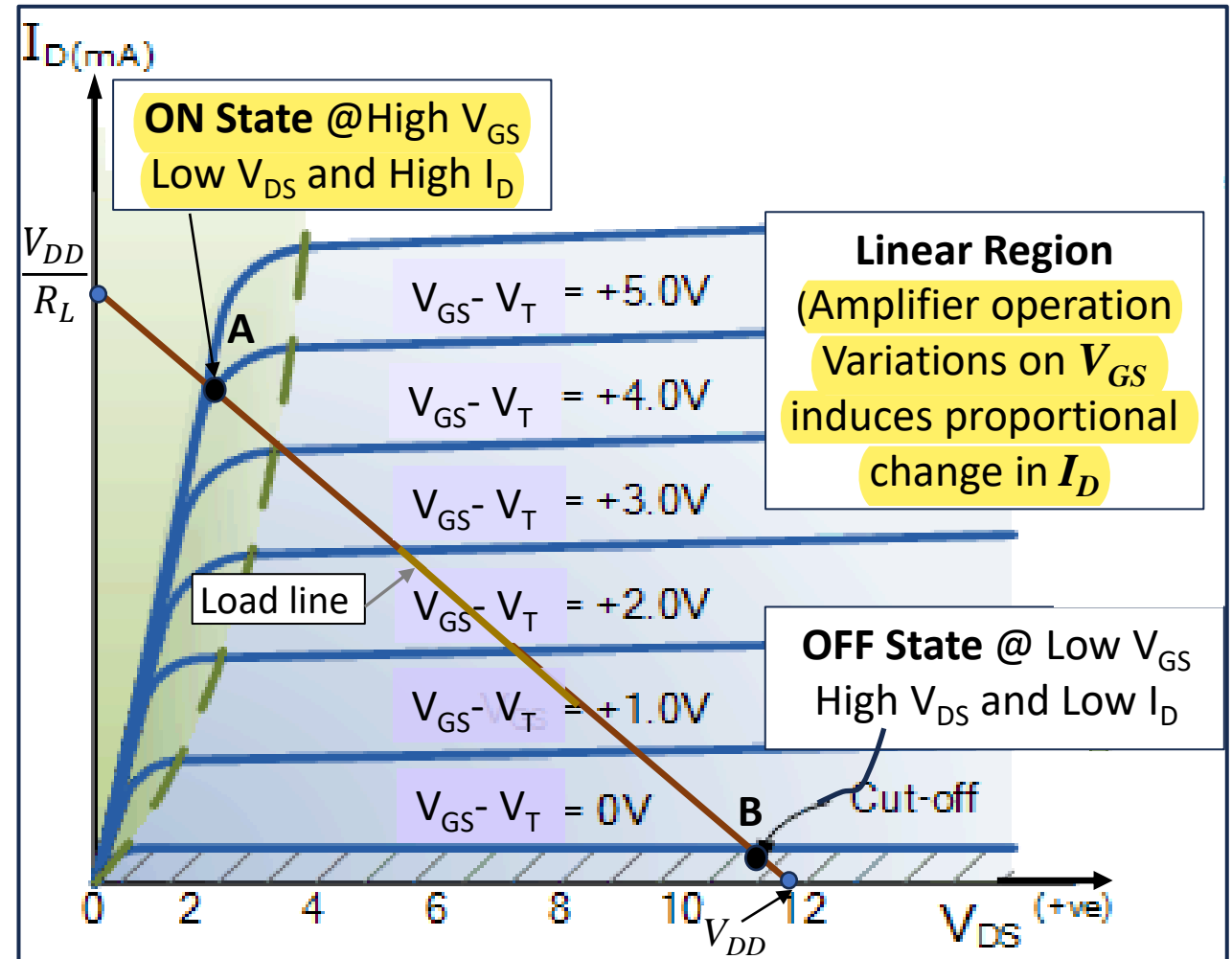- Enhancement MOSFETs start conducting when the channel between the Drain and Source is formed.
- In N-Channel MOSFETs, N-channel is formed.
- $V_T$  is the minimum value of  $V_{GS}$  for the formation of the channel (Hence,  $V_{GS} > V_T$  for MOSFET to be ON)
- $I_D$  increases as  $V_{GS}$  increases further




Typical ' $V_{DS}-I_D$ ' characteristics for N channel Enhancement mode MOSFET  
A & B: operating points for switching action  
The load line between A and B represents Linear region
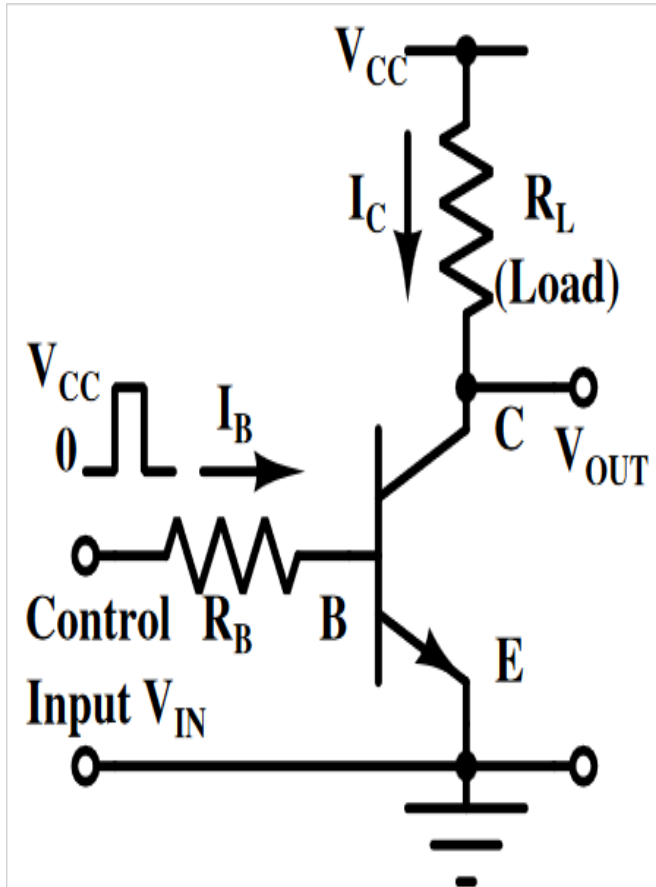
# Switching Transistors with $V_{in}$ as Control Input





$V_{in}$  to control NPN BJT

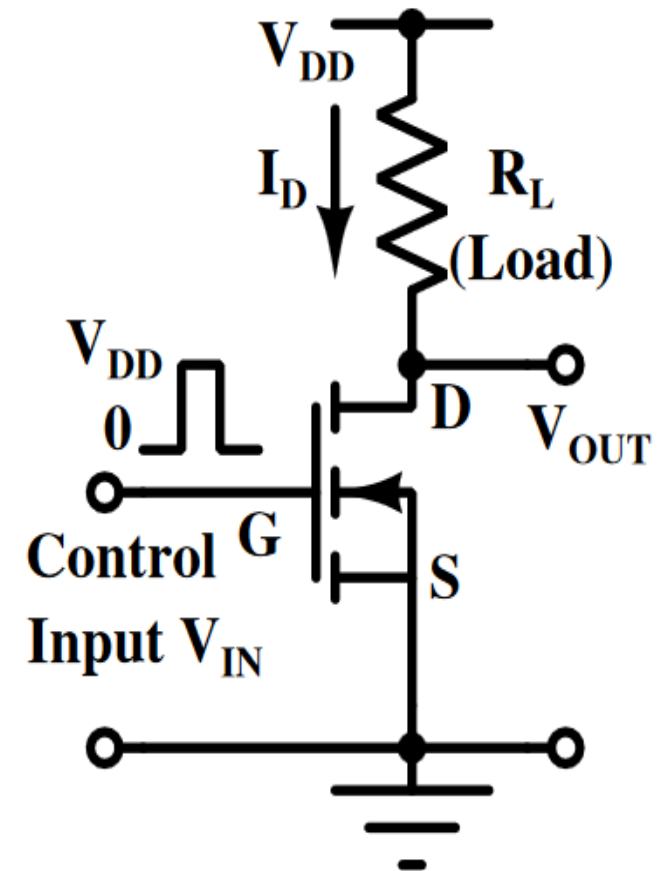

$V_{in}$  to control N-Channel enhancement MOSFET


# Switching Operation for BJT

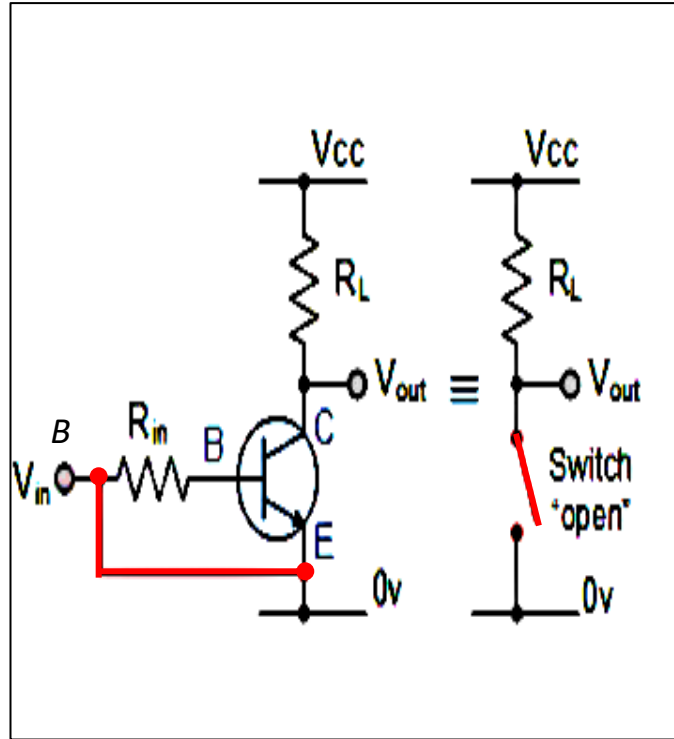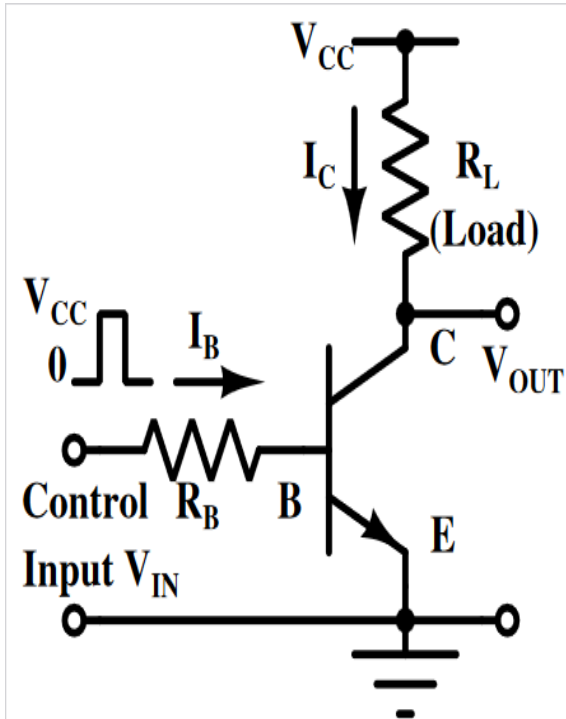

Input Grounded  $\rightarrow I_B \approx 0$ , OFF state.

$$I_C \approx 0 \rightarrow V_{OUT} = V_{CE} \approx V_{CC}$$

Transistor as 'Open Switch'.

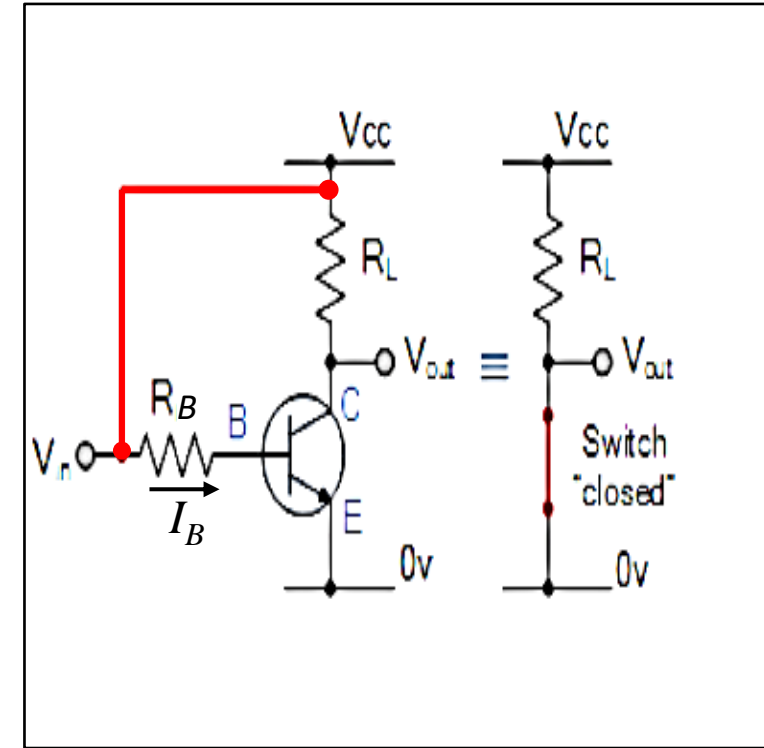


Input connected to  $V_{cc} \rightarrow$  High value of  $I_C$

$$V_{OUT} = V_{CE} \approx 0.2 \text{ V}$$

$$I_B = (V_{CC} - V_{BES}) / R_B, V_{BES} \approx 0.8 \text{ V}$$


Transistor as 'Closed Switch'.
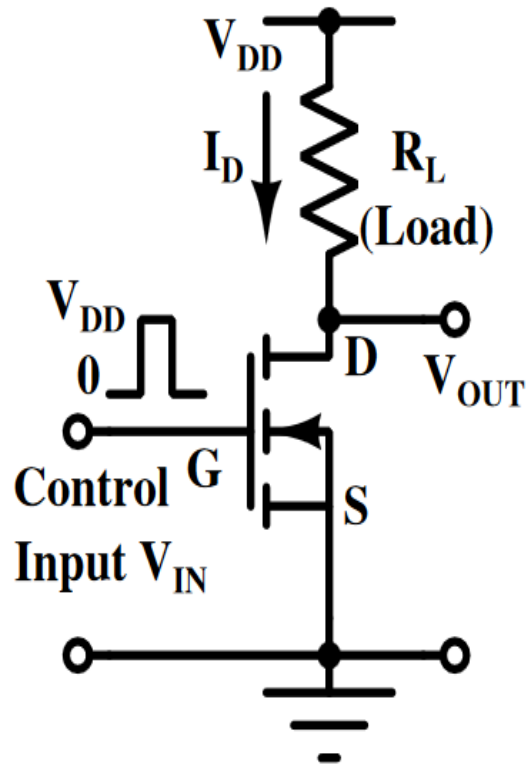
# Switching Operation for N-Channel Enhancement MOSFET



$V_{in}$  to control  
N-Channel MOSFET

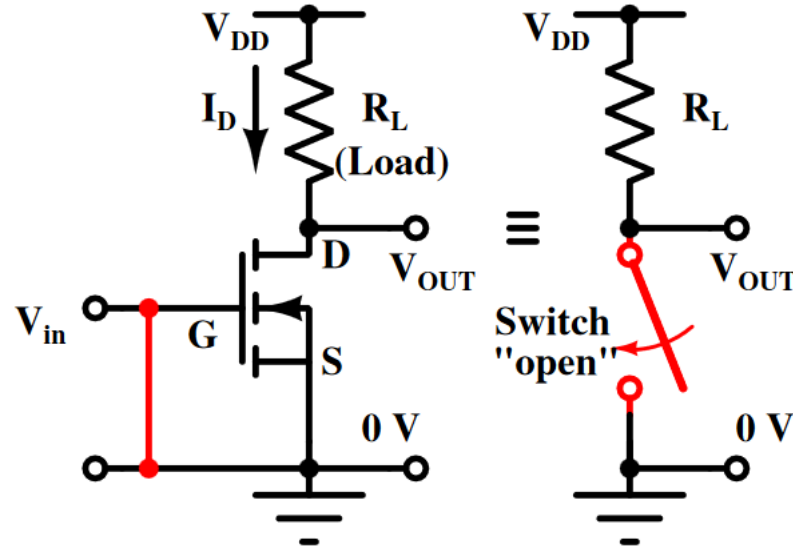Connecting  $V_{in}$  to Ground  $V_{GS} < V_T$




Input Grounded  $\rightarrow V_{GS} = 0$ , OFF state.

$I_D \approx 0 \rightarrow V_{OUT} = V_{DS} \approx V_{DD}$ .

Transistor as 'Open Switch'.

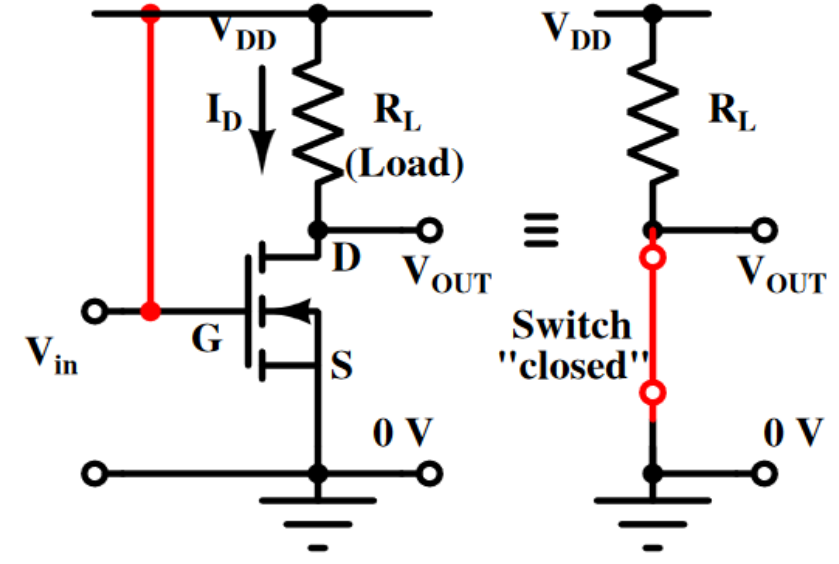Connecting  $V_{in}$  to  $V_{DD} \rightarrow V_{GS} \gg V_T$




Input connected to  $V_{DD} \rightarrow$  High  $I_D$ , ON state.

$V_{OUT} = V_{DS} \approx 0 \text{ V}$  ( $= I_D R_{DS(ON)} = 0.1 \text{ to } 0.8 \text{ V}$ , depending on current &  $R_{DS(ON)}$ ).


Transistor as 'Closed Switch'

# Switching Loads Connected to Supply

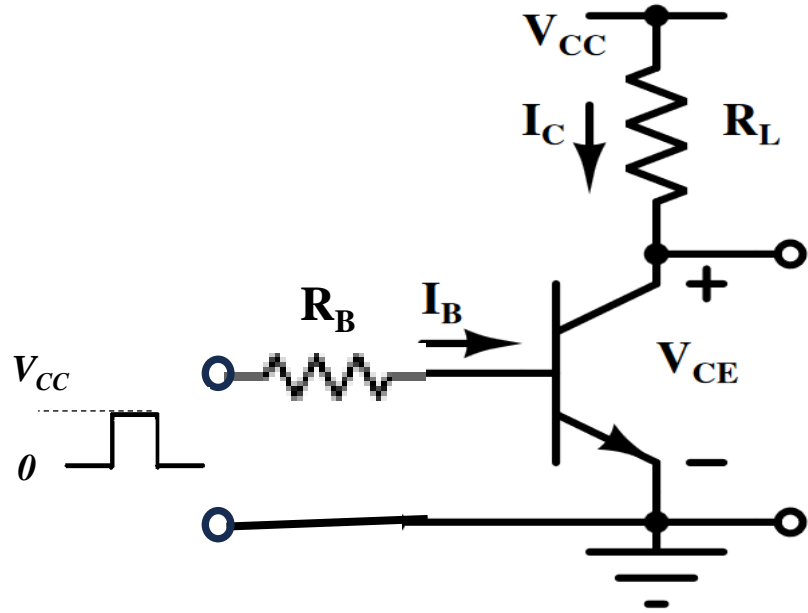



1. Load connected to supply is switched using an NPN transistor OR an N-Channel Enhancement MOSFET.
2. The switch is ON when the control voltage goes to the higher value.

Switching loads using NPN type BJT

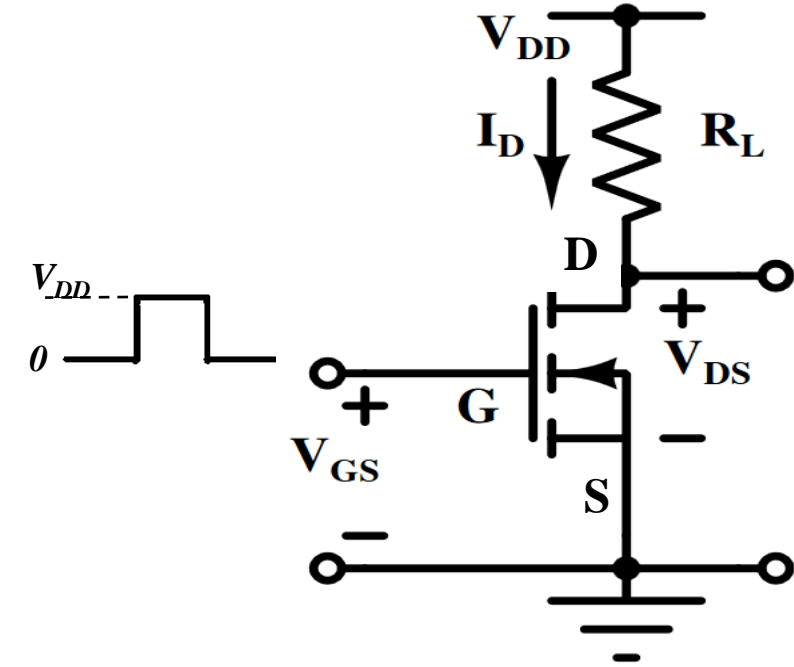


Switching loads using N-Channel MOSFET

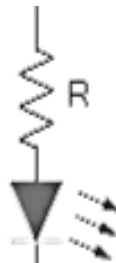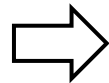Other loads to be switched can be connected in place of the resistor  $R_L$ .



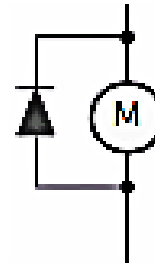
LED Diode Array with Current Limiting Resistor



DC Motors




Heating Element

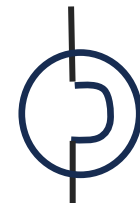

Incandescent Lamp




# Switching Loads Connected to Ground

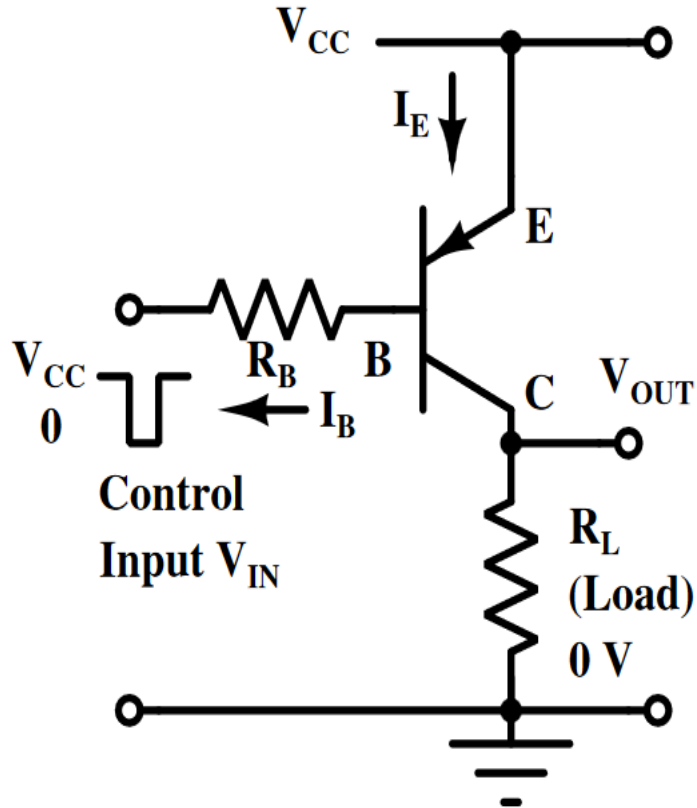

Switching loads using PNP type BJT


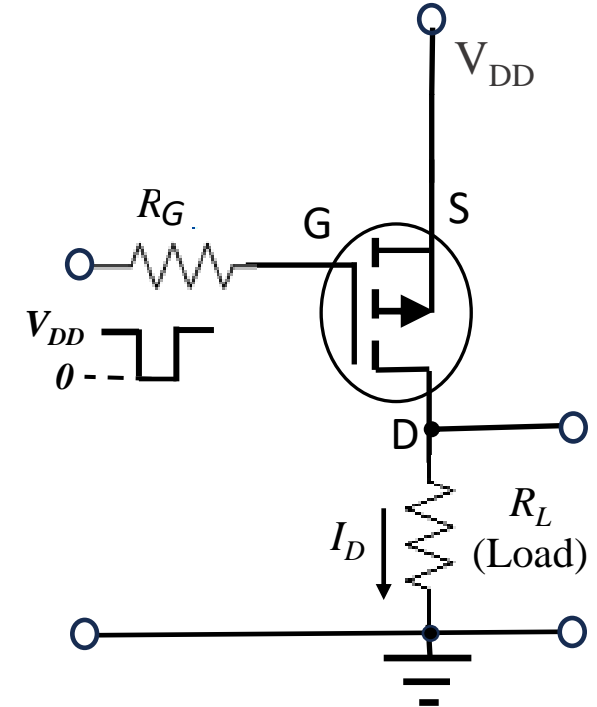
1. Load connected to ground is switched using a PNP transistor OR a P-Channel Enhancement MOSFET.
2. The switch is ON when the control voltage goes to the lower value.



Switching loads using P-Channel Enhancement mode MOSFET
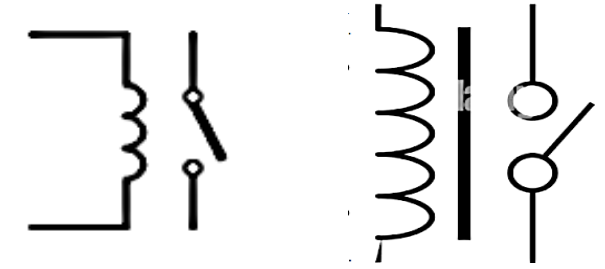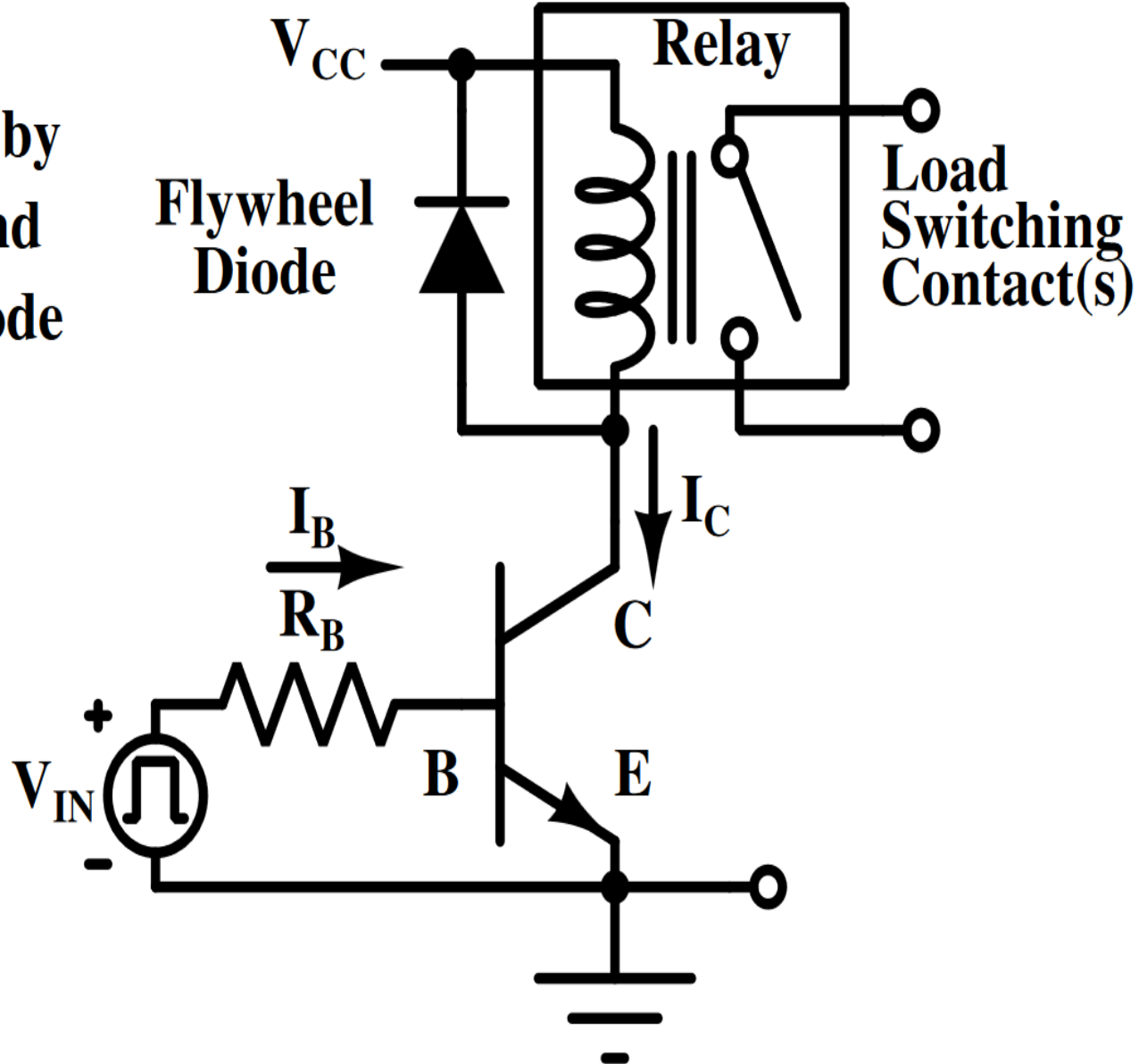
# Relay Operation Using a BJT Switch

$R_L$  replaced by  
Relay coil and  
Flywheel diode




Circuit Symbols for a Relay

By controlling base current ( $I_B$ ) of BJT, high relay coil current ( $= I_C$ ) can be switched.

Current Gain:  $\beta = I_C / I_B$
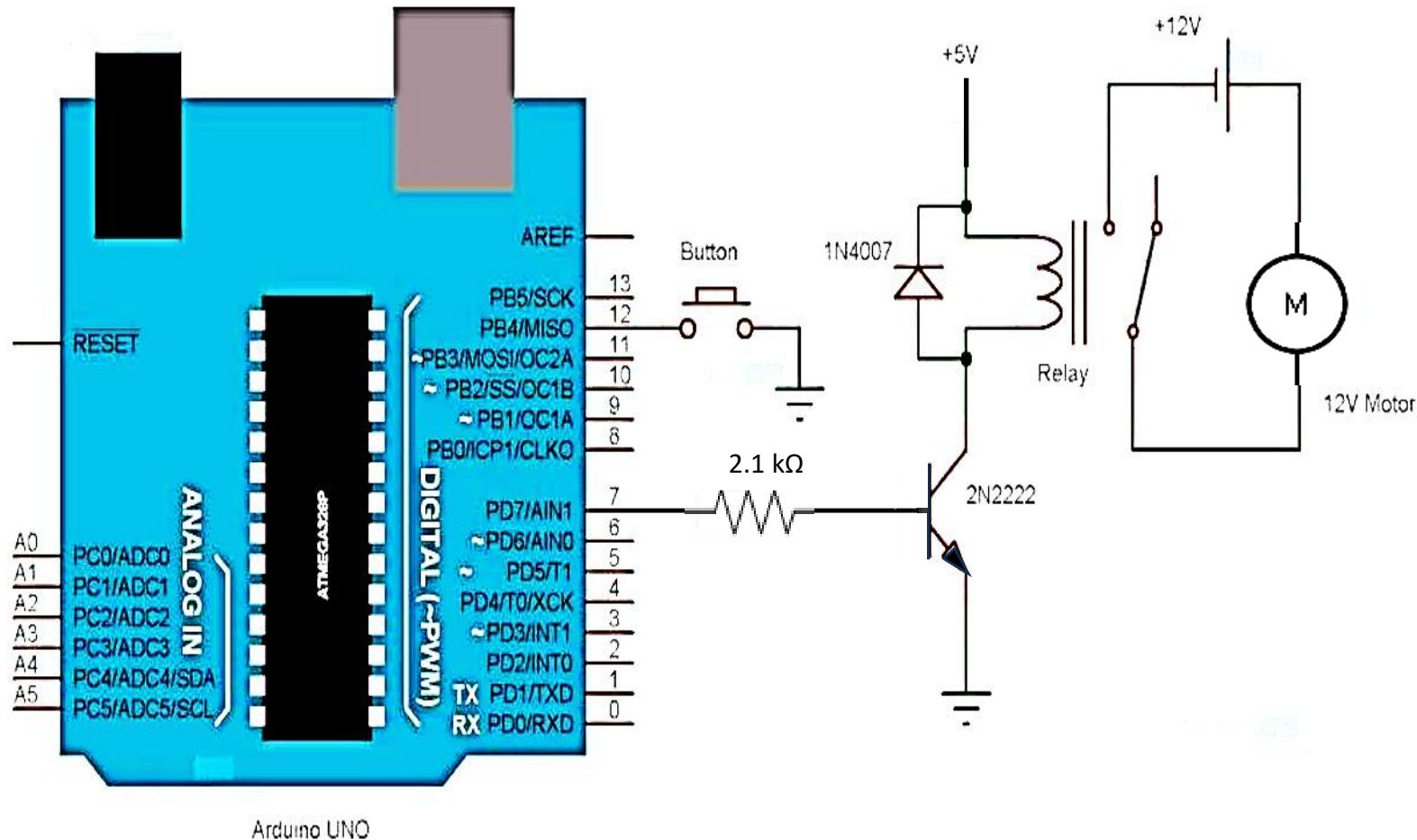
# Relay Switching Using Micro-Controller (Arduino)



Arduino Relay Control Circuit Diagram

Source: <https://www.electronicshub.org/arduino-relay-control/>

This is an example of operating a relay with 'Arduino digital output pin ( PD7 ) and NPN transistor.

Relay Coil Current = **60 mA**,  
Common emitter current gain in saturation mode,  $\beta_{\min} = 30$ .

Action: Set the pin **PD7** to 'Hi'.

This will put the transistor in saturation mode or **ON** state.

This shall allow the current to flow through the relay coil making the relay **ON**.

Base current ( $I_B$ ) required to drive the transistor to ON state is 2 mA.

$$(I_B = I_c / \beta_{\min} = 60 / 30 = 2 \text{ mA})$$

# Questions and Discussions